

19ECE282
DIGITAL ELECTRONICS
AND
SYSTEMS LAB

VENDING MACHINE

TEAM MEMBERS:

CB.EN.U4ECE22141

CB.EN.U4ECE22142

CB.EN.U4ECE22143

Question:

A Vending machine supplies the following beverages: coffee, tea, milk and cocoa. The machine can be accessed only based on a 3-bit login and 2-bit password (only four valid users). If the user is authenticated properly, the machine will assert the following signals: -

(i) coffee OK if coffee is chosen and display the character ‘1’ in a seven segment display.

(ii) tea OK if tea is chosen and display the character ‘2’ in a seven segment display.

(iii) milk OK if milk is chosen and display the character ‘3’ in a seven segment display.


(iv) cocoa OK IF cocoa is chosen display the character ‘4’ in a seven segment display.

(v) The display will show “E” in case of wrong login/password.


USERNAME(3-BIT)/PASSWORD(2-BIT)

<i>USERNAME</i>				<i>PASSWORD</i>	
A	B	C		D	E
0	0	1		0	0
0	1	1		1	1
1	0	1		1	0
1	1	1		0	1

SIMULATION:

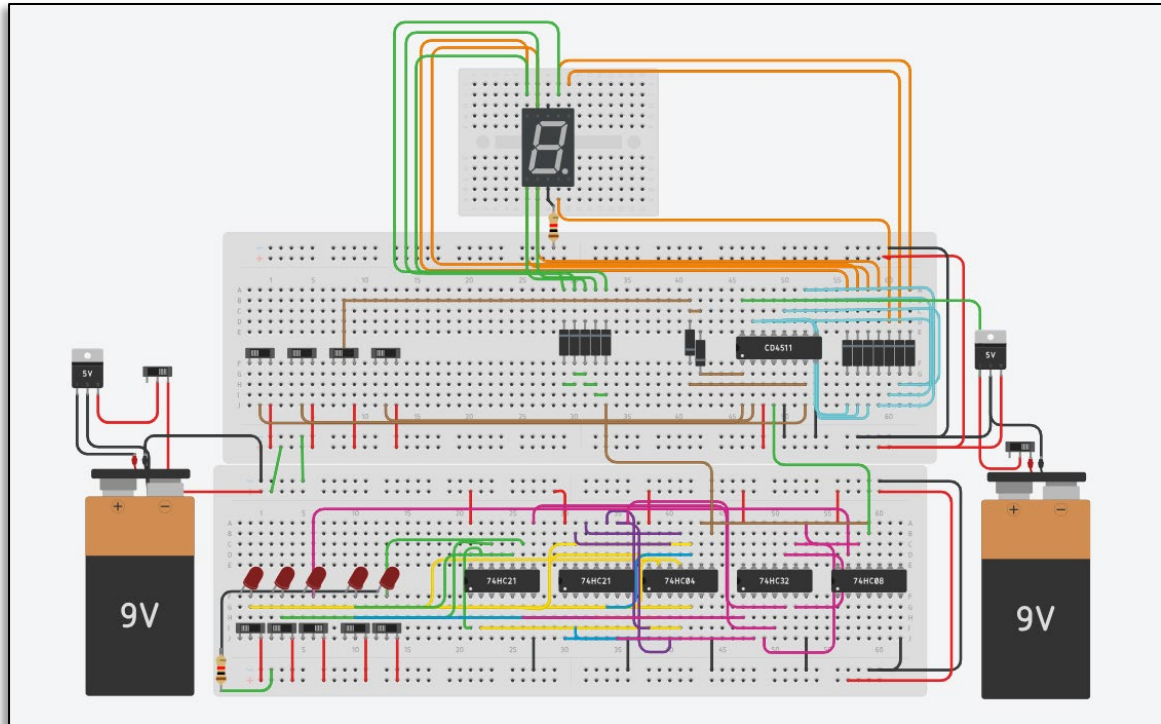


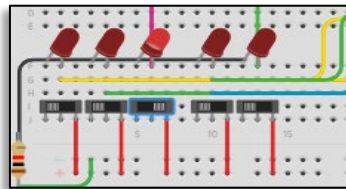When correct login/password is entered: -




Decoder activated; when '**COFFEE**' chosen (switch 1): -


Character '**1**' displayed

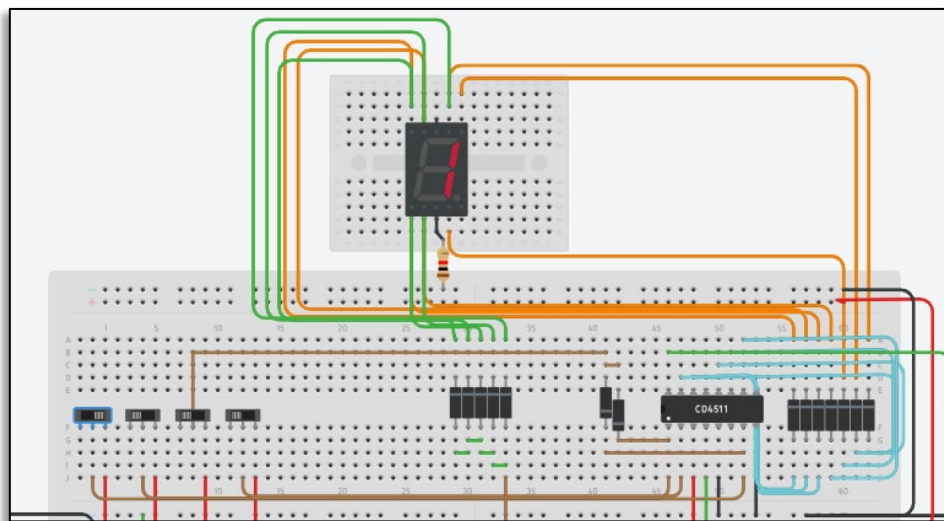

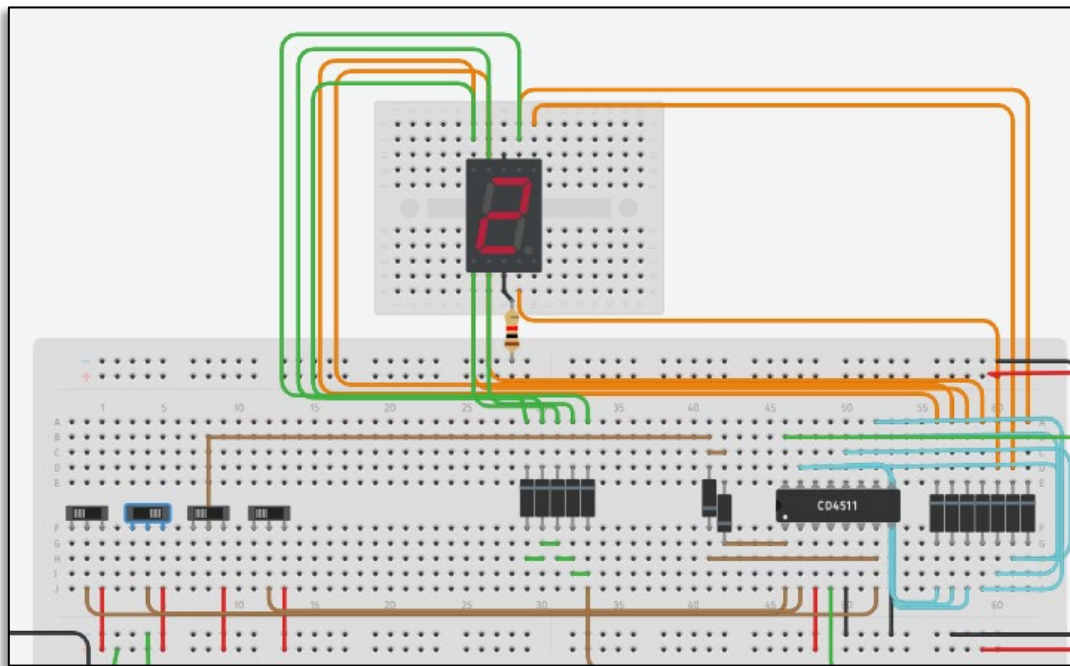
When **TEA** chosen (switch 2): -
Character '2' displayed.



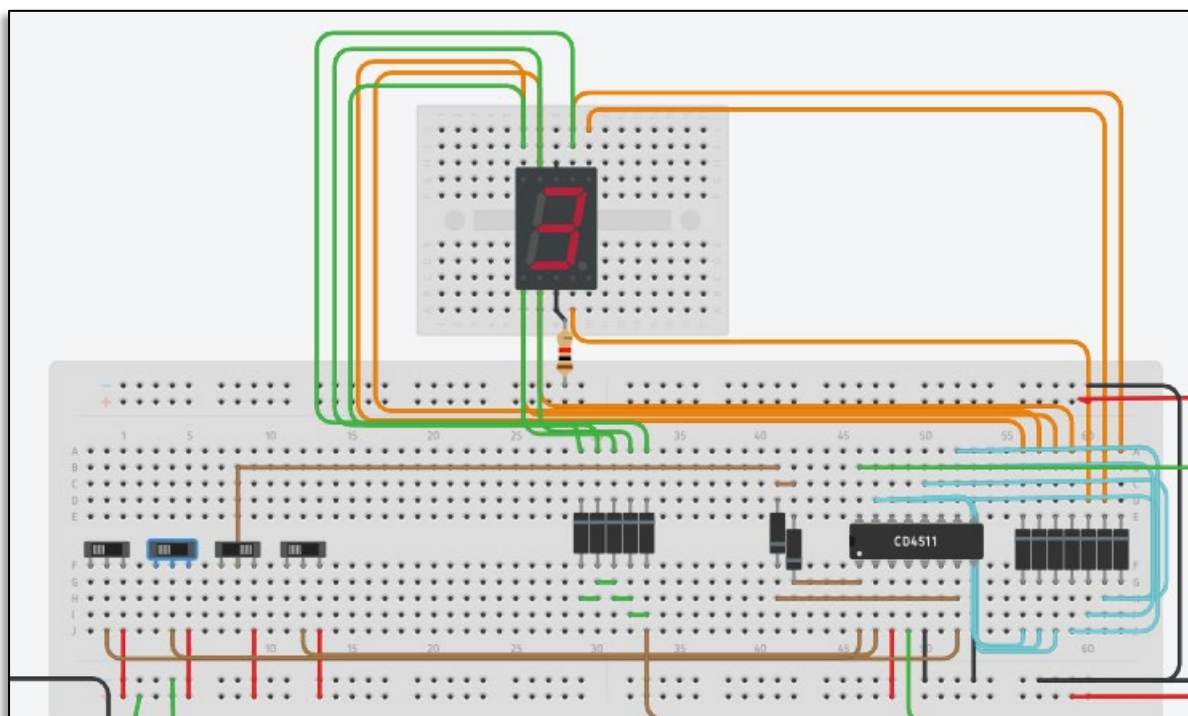
When **MILK** chosen (switch 3): -
Character '3' displayed.



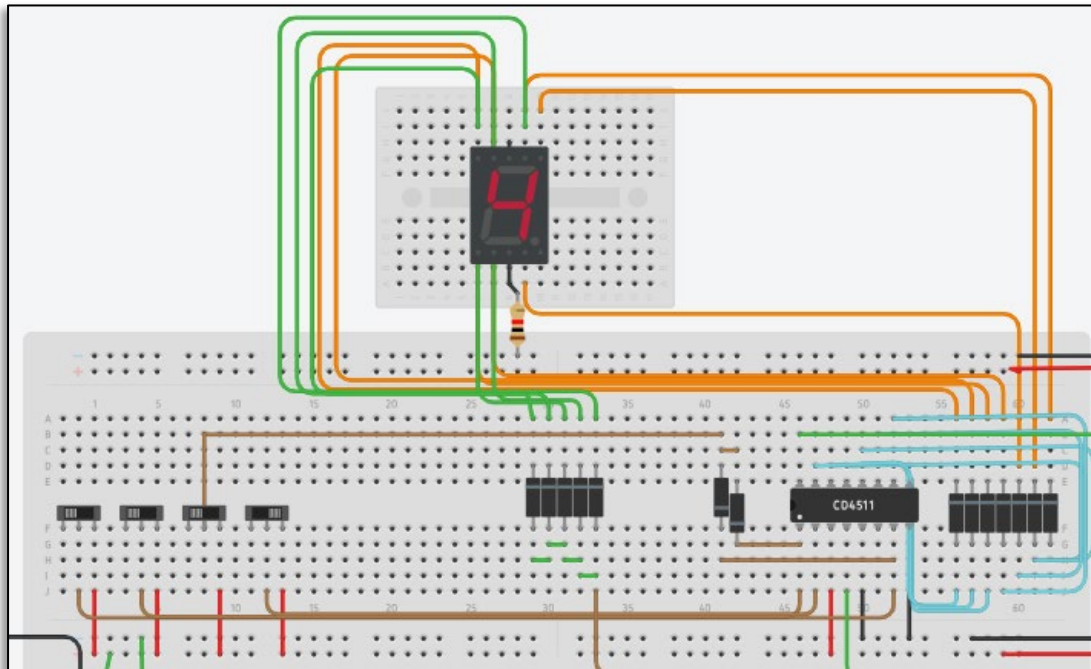
When **COCOA** chosen (switch 4): -
Character '4' displayed.



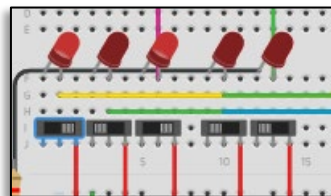When wrong login/password is entered: -
E is displayed.
Wrong input: -




“E” displayed: -

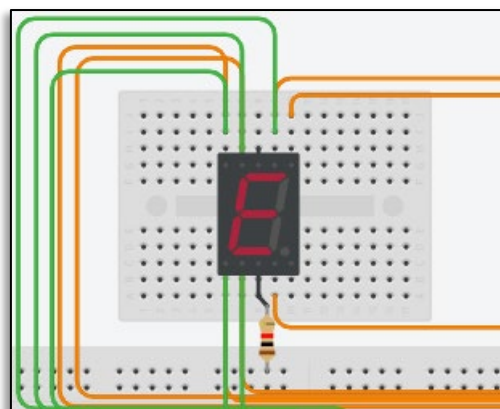


PIN DIAGRAMS:


CD5411 (BCD – 7 SEGMENT DECODER)

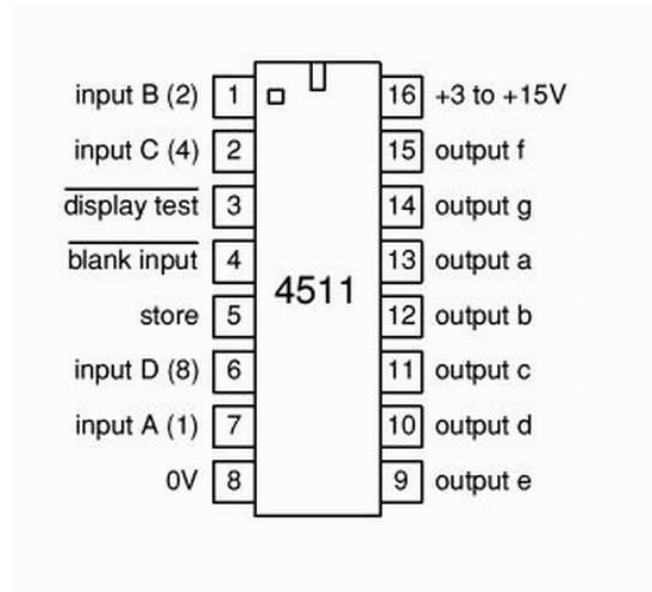


74HC21(DUAL 4-INPUT AND GATE)

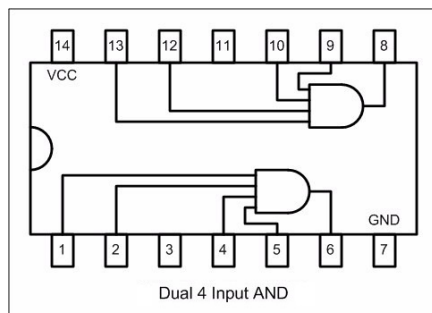

74HC32(QUAD OR GATE)

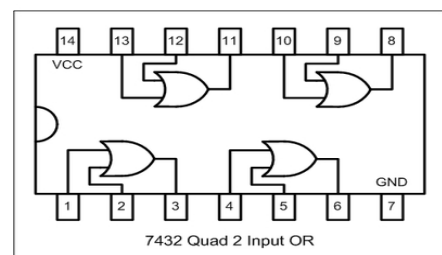

74HC04 (HEX INVERTER) GATE

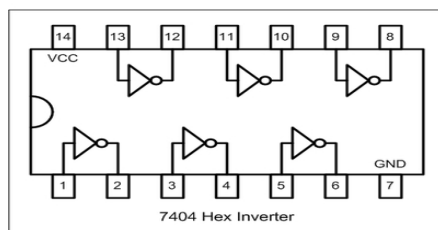

74HC08(QUAD AND GATE)

